

HW6 – The final MIPS

Part I – Adding new instructions

Part II – Adding Data Forwarding

Part III – Adding Branch Forwarding

HW6 – The final MIPS

Part I


Adding **lui**, **ori**, **jr**, **jal** instructions to the CPU instruction set: Rtype, addi, beq, bne, j, lw, sw

HW6 instruction set

(new inst. in red)


R-type

 add Rd, Rs, Rt # Rd=Rs+Rt
 sub Rd, Rs, Rt # Rd=Rs-Rt
 and Rd, Rs, Rt # Rd=Rs AND Rt
 or Rd, Rs, Rt # Rd=Rs OR Rt
 xor Rd, Rs, Rt # Rd=Rs XOR Rt
 slt Rd, Rs, Rt # if Rs<Rt Rd=1 else Rd=0
 jr Rs # PC=Rs (note that Rd=0)



I-type

 addi Rt, Rs, imm # Rt=Rs+ sext(imm)
 lw Rt, imm(Rs) # Rt=M[Rs + imm]
 sw Rt, imm(Rs) # M[Rs + imm]=Rt
 beq Rs, Rt, label # if Rs==Rt, PC=PC+4+ sext(imm)*4
 # else PC=PC+4
 bne Rs, Rt, label # same as beq with cond of Rs≠Rt
 ori Rt, Rs, imm # Rt=Rs OR imm (no sext)
 lui Rt, imm # Rt= imm<<16 (no sext)





j-type

j imm # PC= imm*4 (no sext)
 jal imm # PC= imm*4, \$31=PC+4 (no sext)




HW5_MIPS


HW5_MIPS CPU

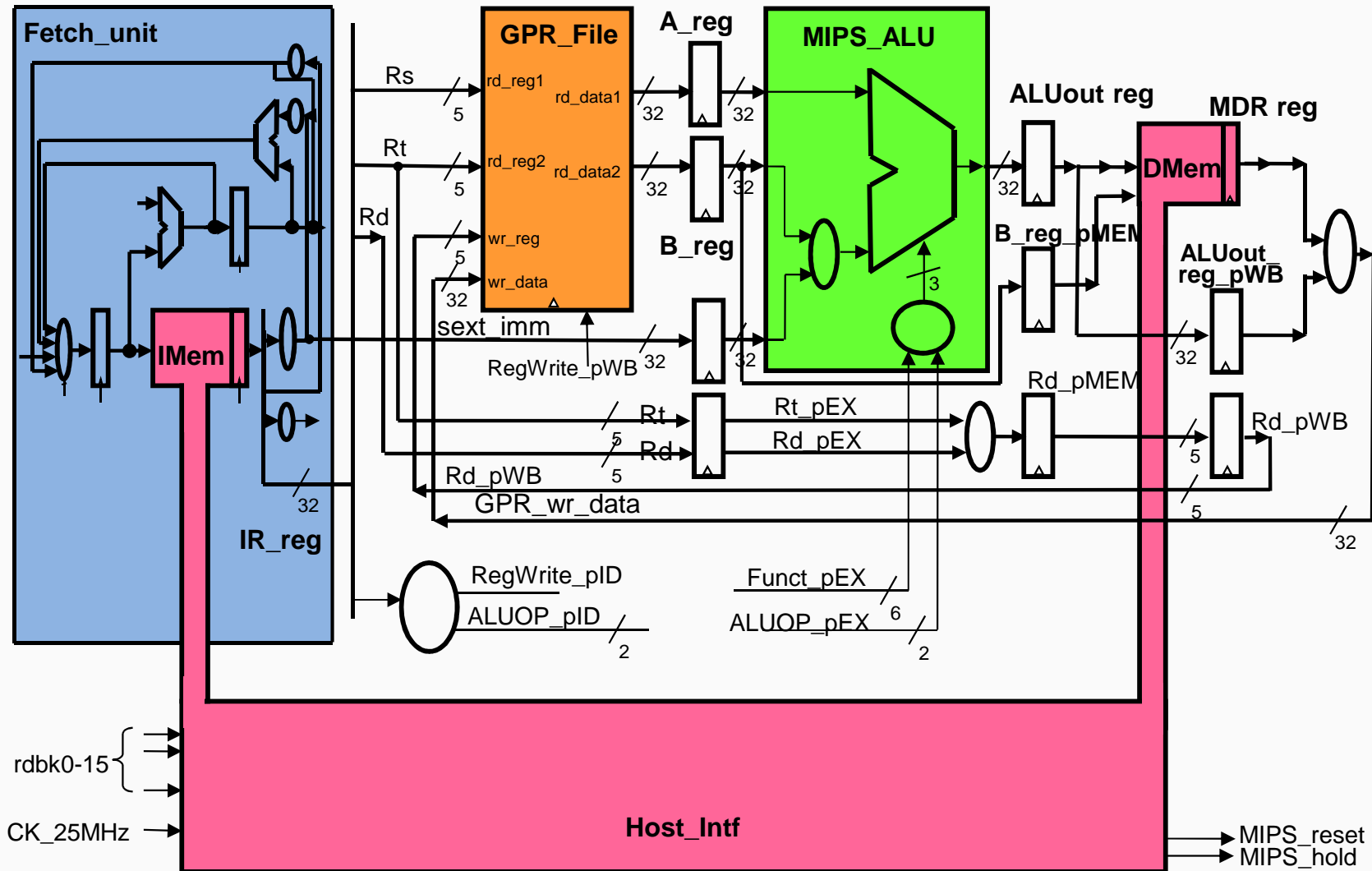 


HW6_MIPS

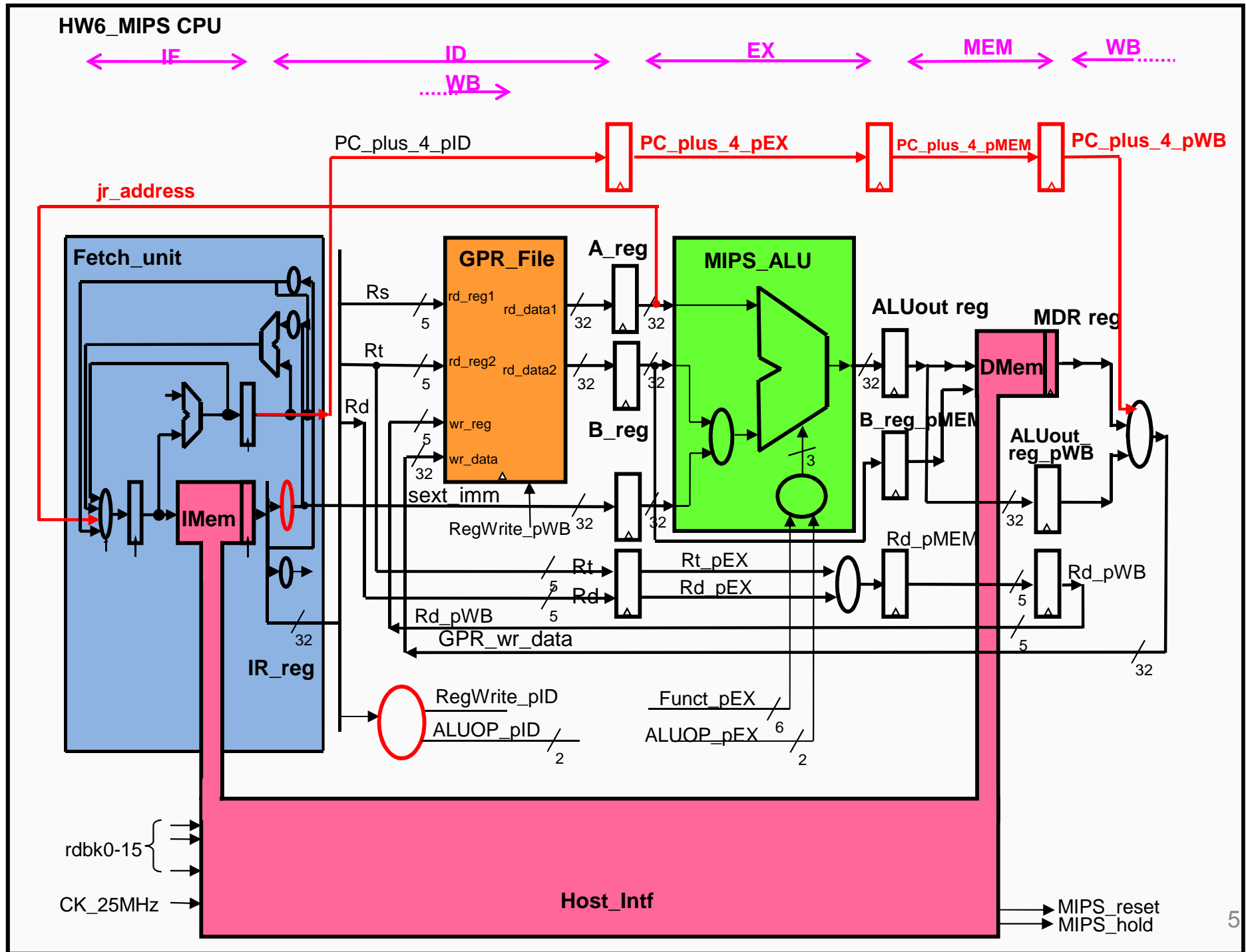


HW6_MIPS

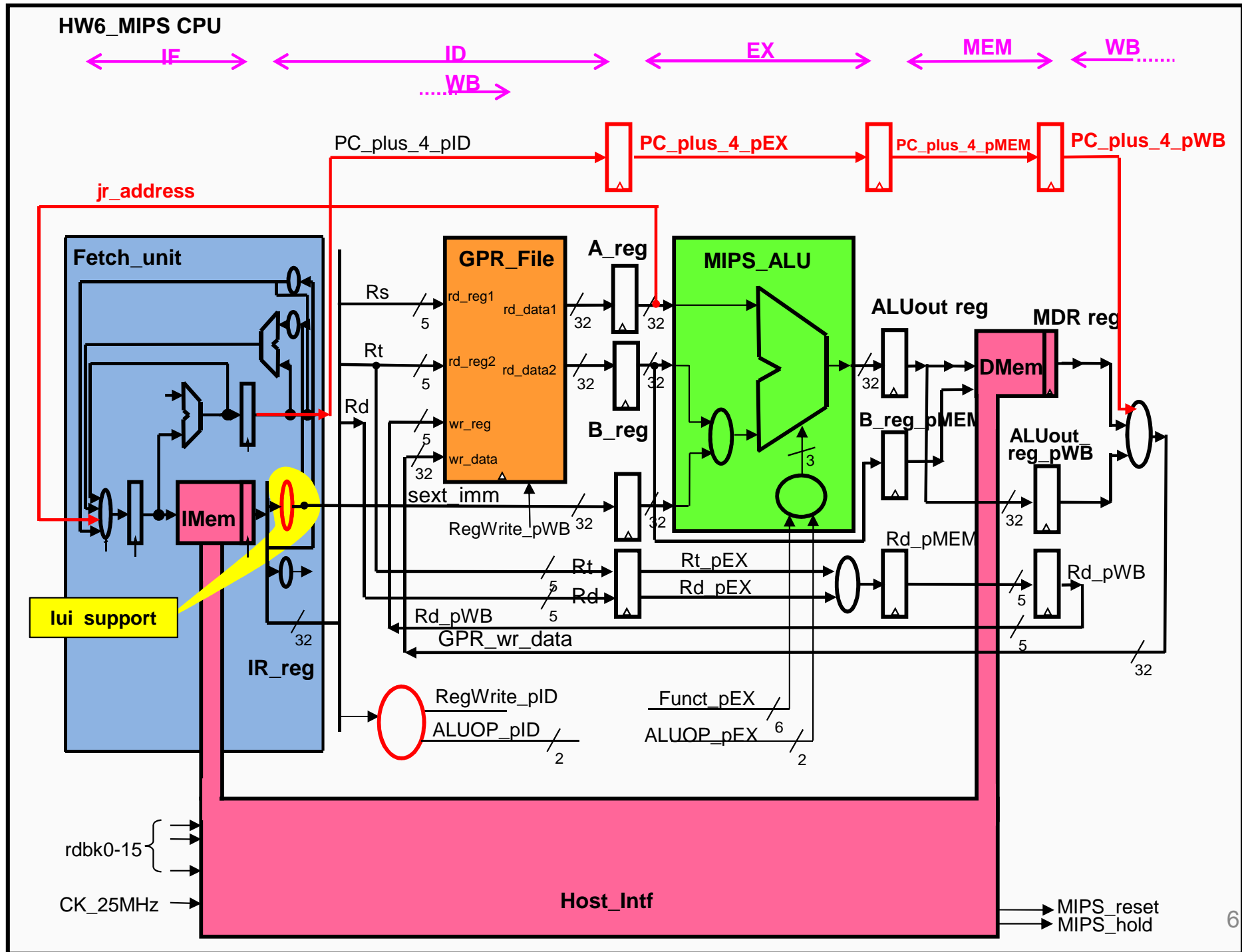


HW6_MIPS

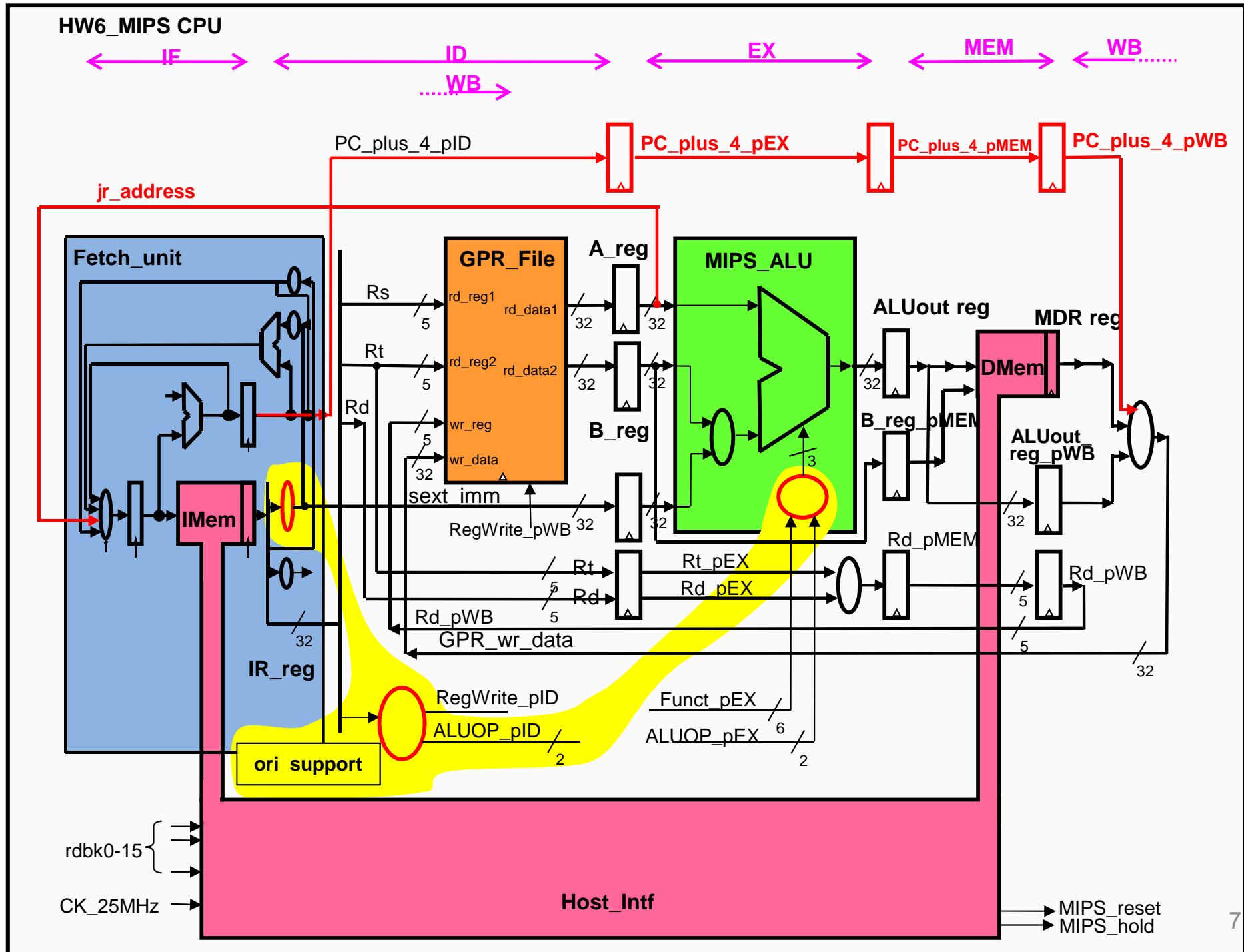

HW6_MIPS

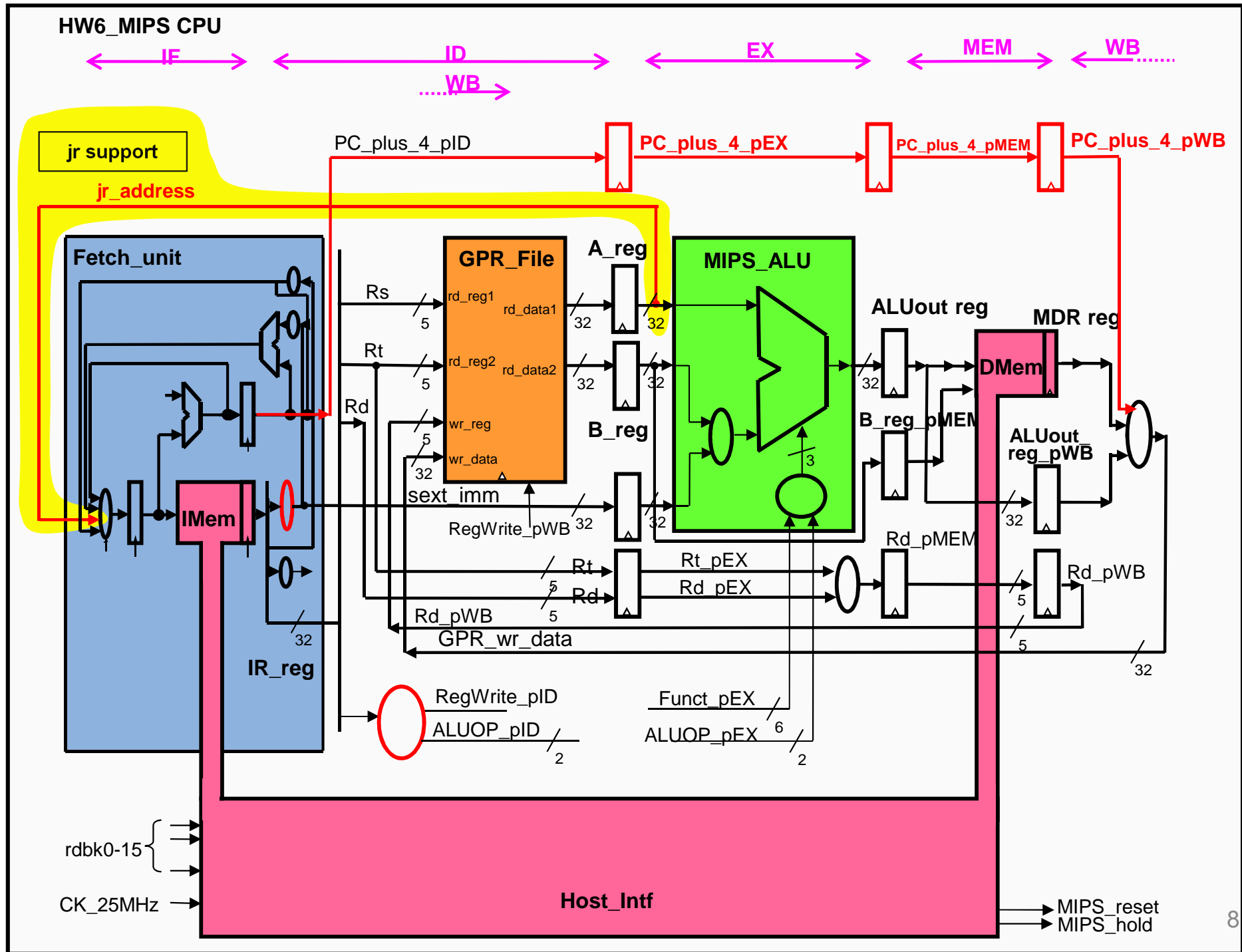

HW6_MIPS

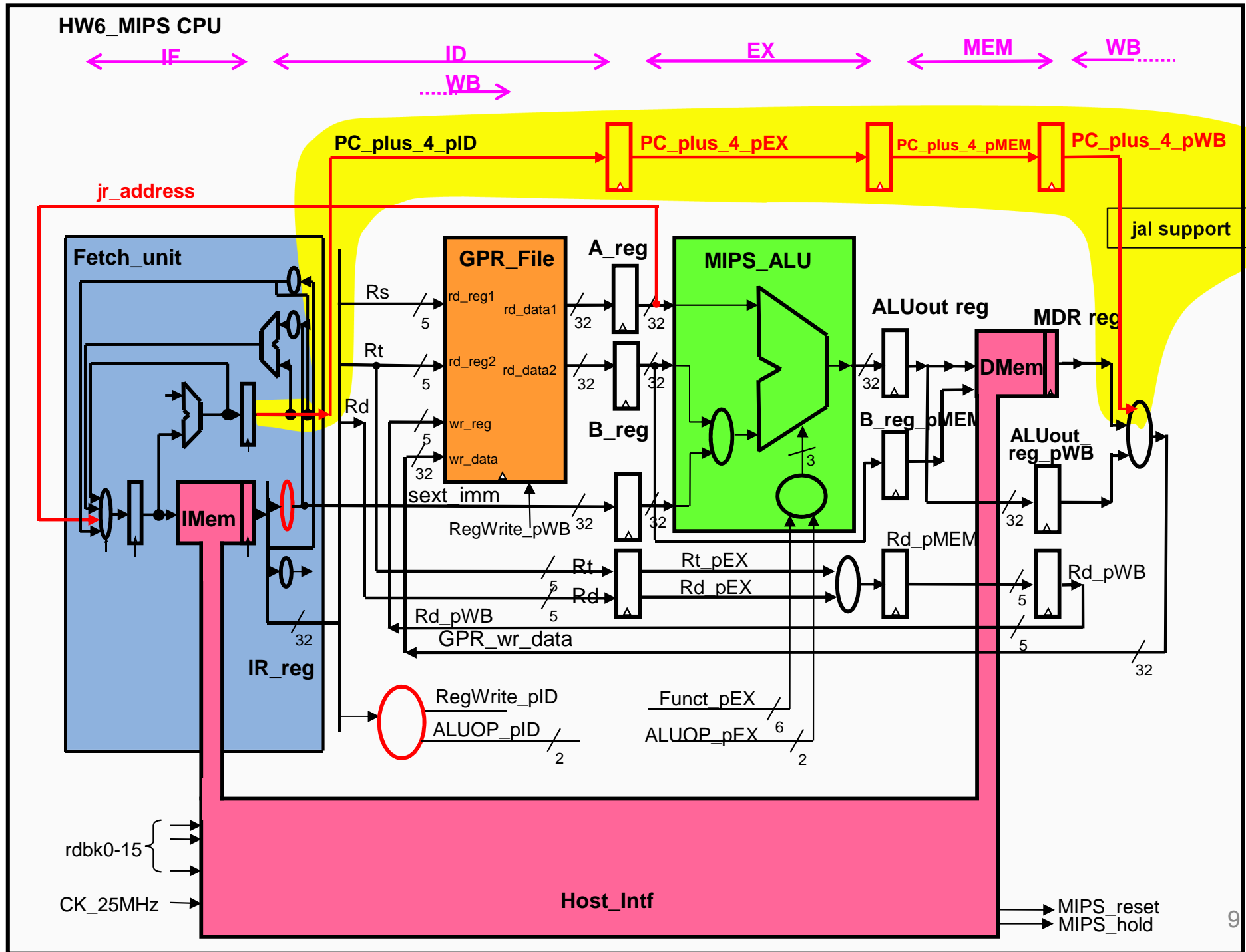

General signals in HW6 MIPS

CK - The 25 MHz clock coming out of the Clock_driver.

RESET – coming out of the Host_Intf and is used as reset signal to all registers

HOLD –coming out of the Host_Intf and is used to freeze writing into all FFs & registers

ID phase signals in HW6 MIPS

IR_reg- a 32 bit register that has the instruction we read from the IMem.

This signal is a rename of the IR_reg_pID signal coming out of the modified Fetch Unit

Opcode – the 6 MSBs of IR_reg. To be decoded and produce the control signals.

Rs – IR[25:21], Rt – IR[20:16], Rd – IR[15:11], Funct – IR[5:0].

sxt_imm – renaming of sxt_imm_pID coming out of the Fetch Unit.

GPR_rd_data1 – the 32 bit output of the rd_data1 of the GPR and input to A_reg.

GPR_rd_data2 – the 32 bit output of the rd_data2 of the GPR and input to B_reg.

Rs_equals_Rt – ‘1’ if GPR_rd_data1== GPR_rd_data2, and ‘0’ otherwise.

Used in branch instructions. That signal (renamed) is sent to the Fetch Unit.

jr_address – connected to the new **jr_adrs_in** pin in the Fetch Unit – for jr inst.

ID control signals in HW6 MIPS - These are created from decoding the opcode:

ALUsrcB – ‘1’ when sxt_imm is used (in addi instruction).

ALUOP – a 2 bit signal. “00” means add(addi inst.), “01” means subtract (not used), “10” will cause the ALU to follow the Funct field.

RegDst – ‘0’ when we WB according to Rt (addi inst.) ‘1’ -according to Rd (Rtype inst.).

RegWrite – ‘1’ when we WB (Rtype or addi inst.), ‘0’ when we don’t (j, beq & bne inst.)

MemWrite – ‘1’ in sw (writing to Dmem), MemToReg = ‘1’ in lw (reading from DMem)

JAL – ‘1’ in jal . Used to control the expanded MemToReg mux

EX phase signals in HW4 MIPS

A_reg – a 32 bit register receiving the GPR_rd_data1 signal. Its value is used in EX phase

B_reg – a 32 bit register receiving the GPR_rd_data2 signal

sext_imm_reg – a 32 bit register receiving the sext_imm coming from the Fetch Unit

Rt_pEX – Rt delayed by 1 clock cycle

Rd_pEX – Rd delayed by 1 clock cycle

ALUoutput – a 32 bit signal of the output of the ALU (renaming of ALU_out signal coming out of the MIPS_ALU component).

PC_plus_4_pEX – PC_plus_4_pID delayed by 1 clock cycle – for jal

EX phase control signals in HW4 MIPS

ALUsrcB_pEX – ALUsrcB delayed by 1 clock cycle.

Funct_pEX – Funct delayed by 1 clock cycle.

ALUOP_pEX – ALUOP delayed by 1 clock cycle.

RegDst_pEX – RegDst delayed by 1 clock cycle.

RegWrite_pEX – RegWrite delayed by 1 clock cycle.

MemWrite_pEX – MemWrite delayed by 1 clock cycle.

MemToReg_pEX – MemToReg delayed by 1 clock cycle.

JAL_pEX – JAL delayed by 1 clock cycle.

MEM phase signals in HW5 MIPS

B_reg_pMEM – a 32 bit register receiving the B_reg signal (i.e., B_reg delayed by 1 CK). This register has the data to be written into the DMem in sw instruction.

Rd_pMEM – the output of RegDest mux – to which reg the CPU writes in the WB phase.

PC_plus_4_pMEM – PC_plus_4_pEX delayed by 1 clock cycle – for jal

MEM phase control signals in HW5 MIPS

MemWrite_pMEM - MemWrite_pEX delayed by 1 clock cycle.

MemToReg_pMEM – MemToReg_pEX delayed by 1 clock cycle.

RegWrite_pMEM – RegWrite_pEX delayed by 1 clock cycle.

JAL_pMEM – JAL_pEX delayed by 1 clock cycle.

WB phase signals in HW5 MIPS

MDR_reg- a 32 bit register that has the data read from the memory. Rename of DMem_rd_data signal coming out of the HW5_Host_Intf_4sim component.

ALUout_reg_pWB - a 32 bit register that has the ALUout_reg data delayed by 1 CK cycle.

GPR_wr_data - a 32 bit signal that is the output of the MemToReg mux

Rd_pWB – Rd_pMEM delayed by 1 clock cycle.

PC_plus_4_pWB – PC_plus_4_pMEM delayed by 1 clock cycle – for jal

WB phase control signals in HW5 MIPS

MemToReg_pWB – MemToReg_pMEM delayed by 1 clock cycle

RegWrite_pWB – RegWrite_pMEM delayed by 1 clock cycle.

JAL_pWB – JAL_pMEM delayed by 1 clock cycle.

You get a **HW6_MIPS_4sim-empty.vhd** file in which you have all of these signals defined . You have to add your design of the HW6_MIPS, i.e., write the equations of the top file. In this vhd file we use the **Fetch_Unit**, **GPR**, **MIPS_ALU**, **Clock_Driver** and the **HW6_Host_Intf_4sim**.

Description of the HW6_MIPS_4sim project

1. **HW6_MIPS_4sim.vhd** – This is your design of HW5. It uses the **GPR**, the updated **MIPS_ALU**, the updated **Fetch_Unit**, the **Clock_driver** and the **HW6_Host_Intf_4sim** components and all of the signals described in 2b.
2. **GPR.vhd** – your GPR File design you prepared in HW3.
3. **dual_port_memory.vhd** – part of the GPR File design you prepared in HW3.
4. **MIPS_ALU.vhd** – your MIPS_ALU design you prepared in HW3 **and updated for HW6!!**
5. **Fetch_Unit.vhd** - The Fetch Unit you prepared in HW2 after the modifications detailed in HW4 **and now in HW6!!**
6. **Clock_driver_for_sim.vhd** – the CK divider & driver we use for simulation (also good for the Modelsim simulator)
7. **HW6_Host_Intf_4sim.vhd** – The prepared components including the IMem and “pre-loaded” program and creating the reset & ck signals.
8. **HW6_TB_for_students.vhd** - The TB vhd file prepared in advance. See the note in 9 below.
9. **HW6_TB_no_fwdng.dat** – this is a data file prepared in advance that is read by the HW6_TB and used to compare the simulation results to the expected ones. Rename it to **HW6_TB_data.dat** or fix the name in the TB

NOTE: Inside the test bench, **HW6_TB_for_students.vhd**, we specified the **path** of the **dat** file. You should update that according to your simulation project actual path.

Simulation report

Y. It should have **four** directories/folders. The first is called **Simulation1**, the 2nd is called **Simulation2**, the 3rd is called **Simulation 3**, the 4th is called **Implementation**. In the Simulation folders you will have 3 sub-folder of:

- **Src_4sim** – here you put all of the *.vhd sources for simulation
- **Sim** – here you should have the HW6_4sim project created by the simulator you used
- **Docs** – Here you put your simulation report. The first few lines in the report will have your ID numbers (names are optional). See the instructions below for the rest of the simulation report.

Simulation1 will have the “**no forwarding**” design of **part I** where you add the lui, ori, jr and jal instructions. You should answer the questions in **Appendix A** and insert these to your report of **Simulation1**.

Simulation report (cont.)

Simulation2 will have the “data forwarding” design of part II where you add the data forwarding to the design of **Simulation1**. You should answer the questions in **Appendix B** and insert these to your report of **Simulation2**.

Simulation3 will have the “branch forwarding” design of part III where you add Branch Forwarding to the design of **Simulation2**. You should answer the questions in **Appendix C** and insert these to your report of **Simulation3**.

Later, in the Implementation phase you will add 2 sub-folders to the **Implementation** folder.

These will be:

Src_4ISE – here you put all of the *.vhd sources and the *.ucf file (and no TB file)

ISE – here you should have the HW6_MIPS project created by the Xilinx ISE SW.

HW6 – The final MIPS

Part II

Adding Data Forwarding

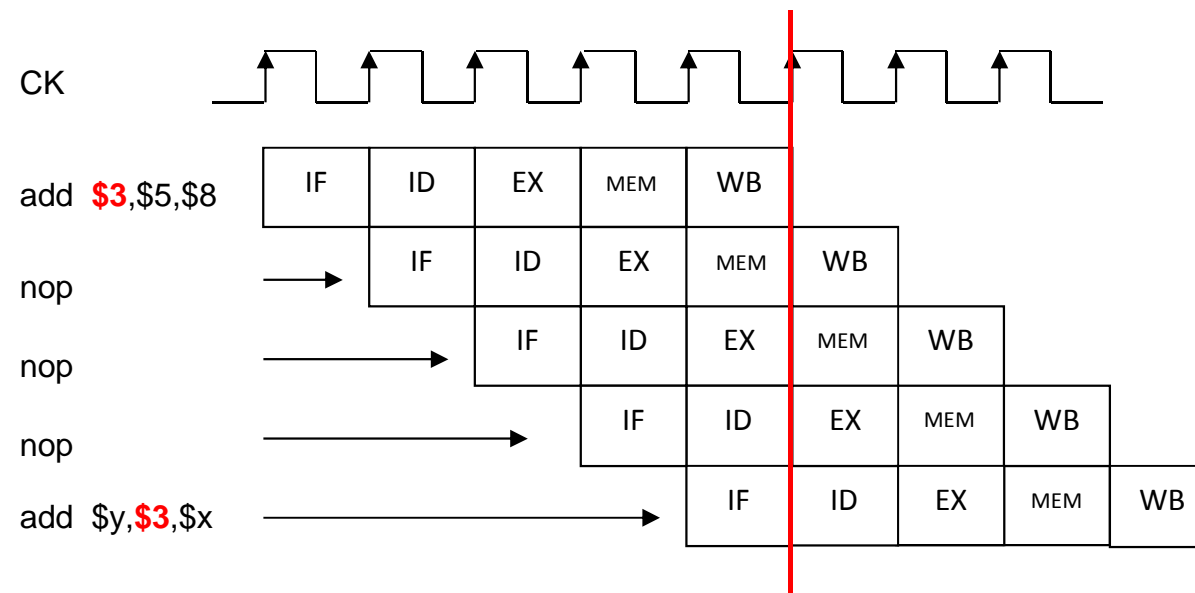


Fig. 2 – The pipelined MIPS latency

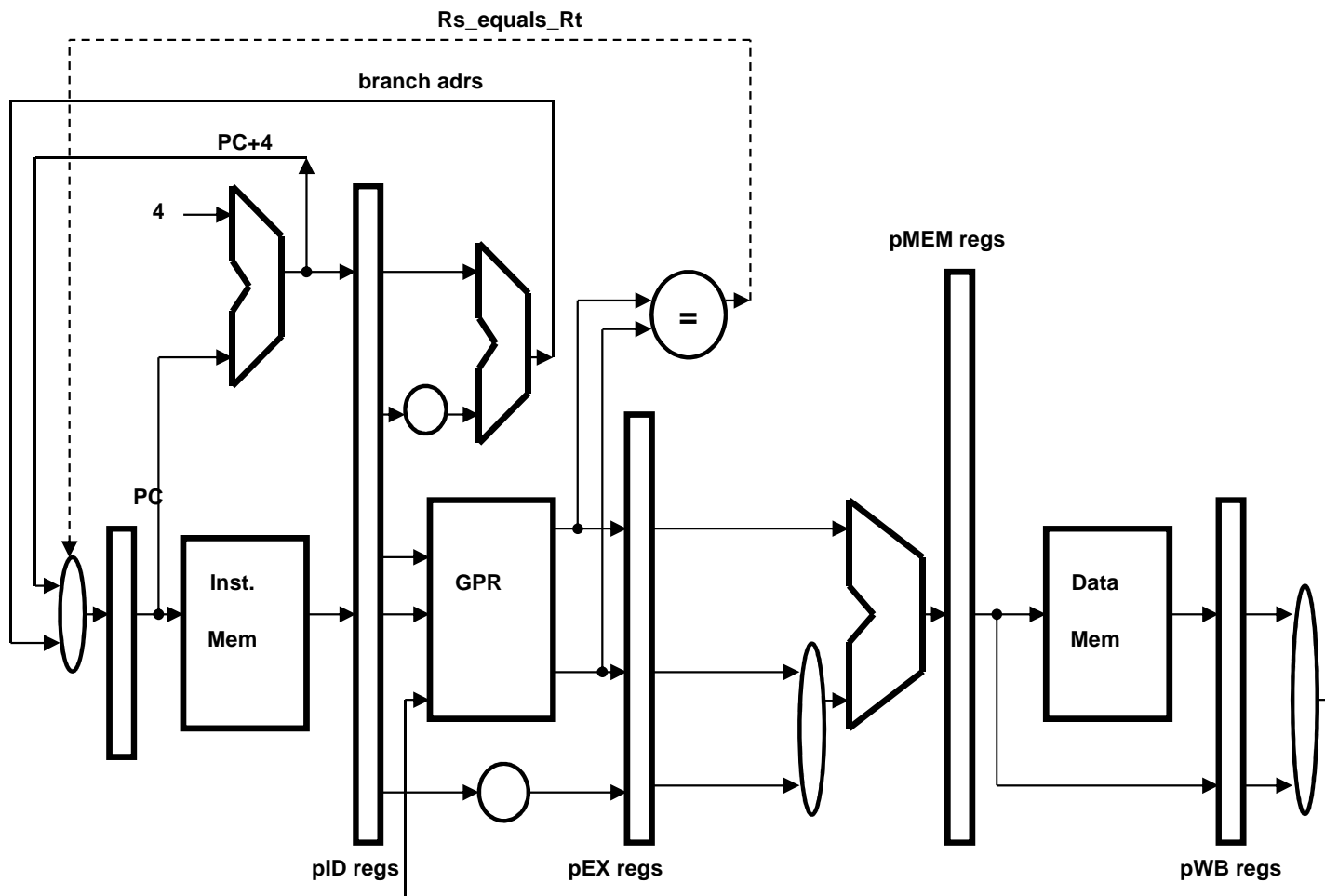


Fig. 4 – MIPS data path (part) with no forwarding

 


Fig. 5 – MIPS Data Path with Data Forwarding

You need to add the **red** signals

You need to handle also the B_reg_pMEM. To which signal should we connect it to?

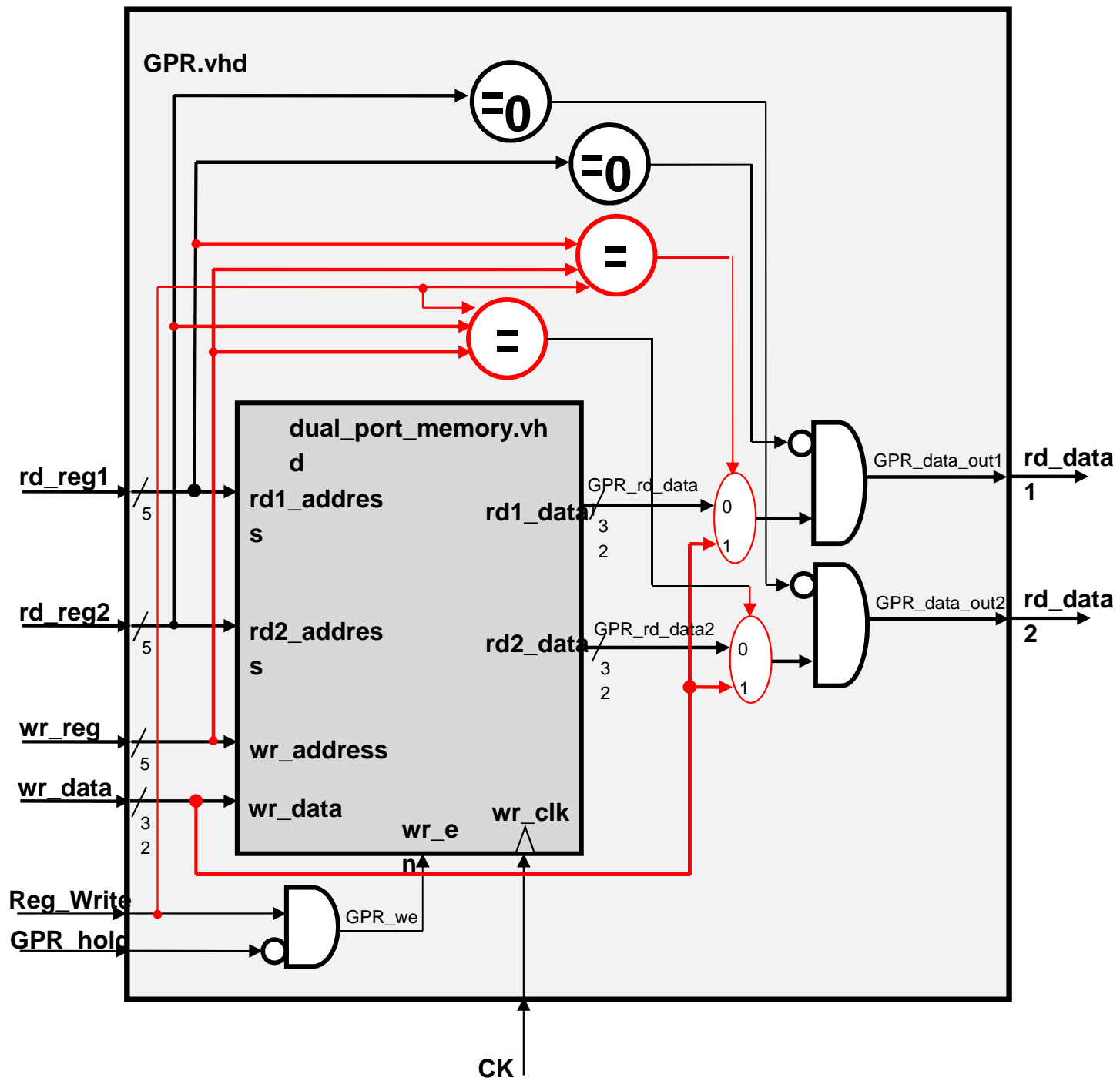


Fig. 6 – MIPS Data Path with Data Forwarding


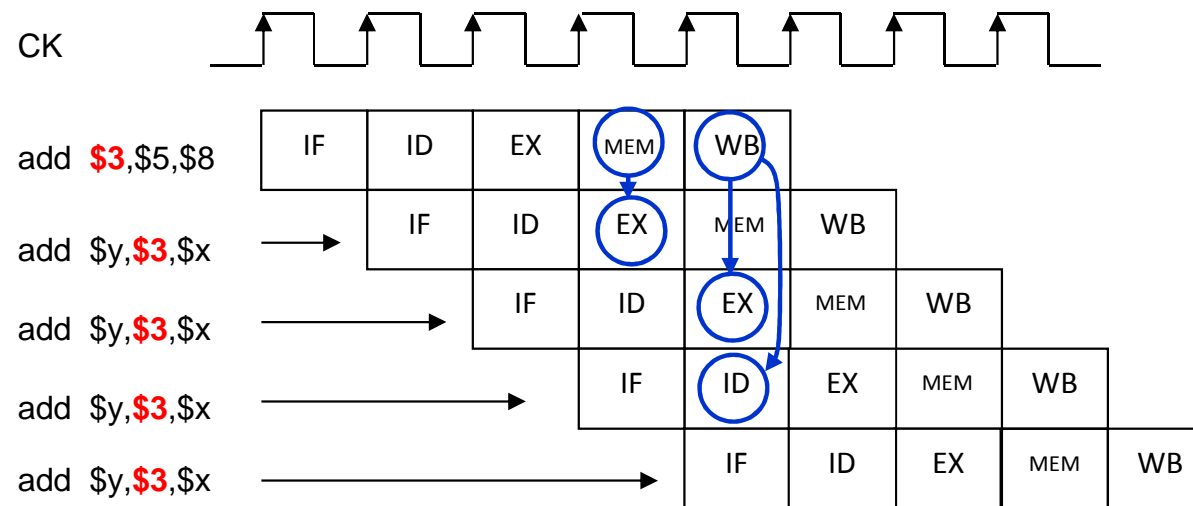


Fig. 3 – Data Forwarding timing diagram
(from the 1st instruction to future instructions)

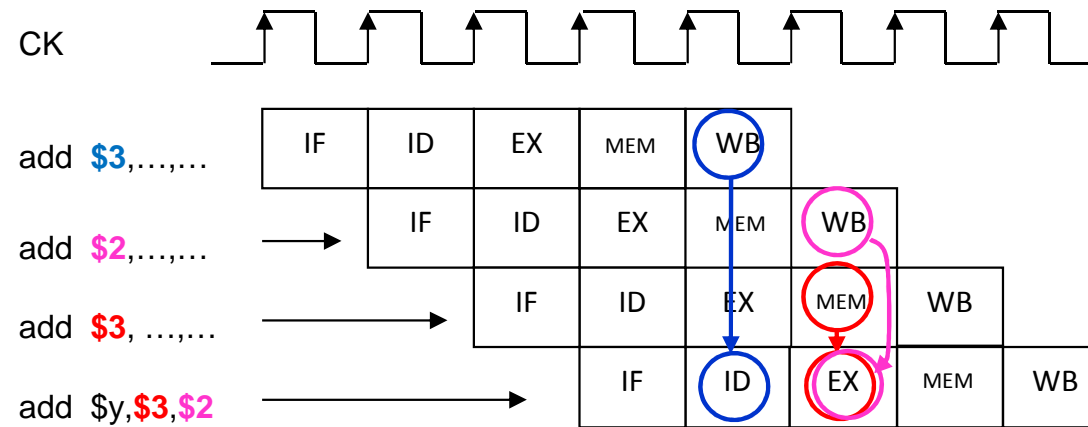

**Fig. 3B – The 3 Data Forwarding options to an instruction
(to the 4th instruction from previous instructions)**

HW6 – The final MIPS

Part III

Adding Branch Forwarding

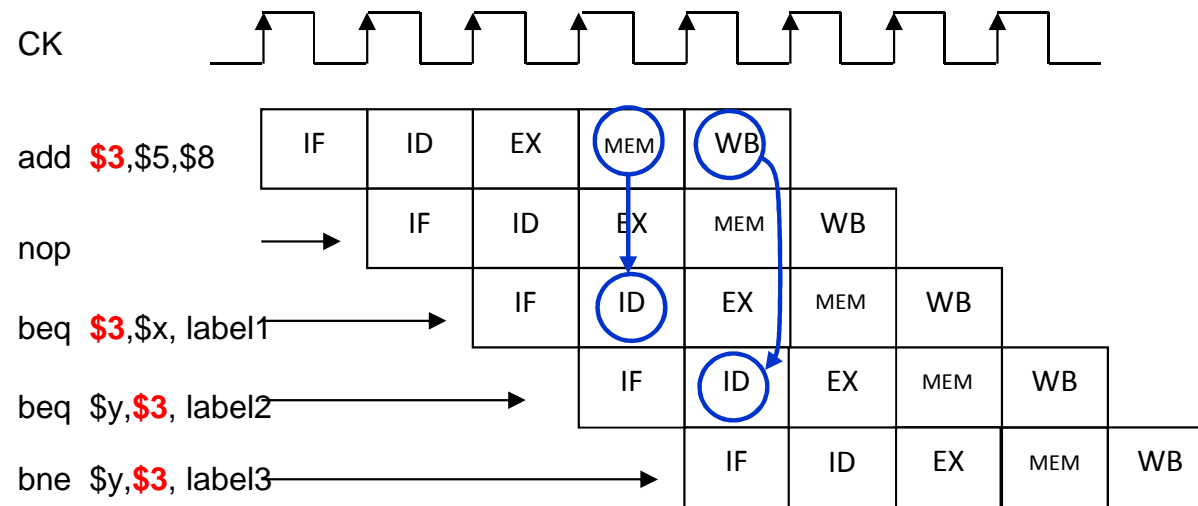


Fig. 7 – Branch Forwarding timing diagram

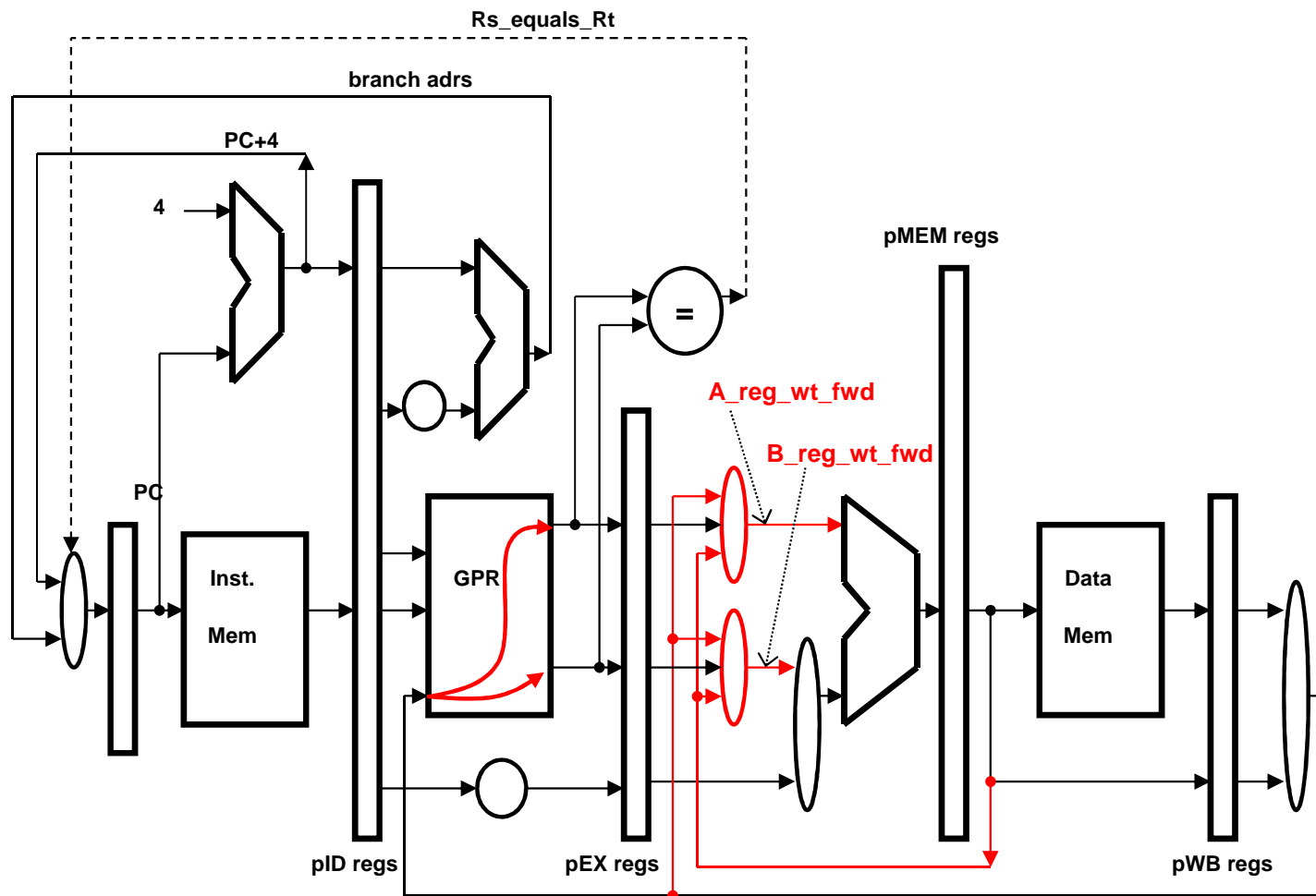


Fig. 5 – MIPS Data Path with Data Forwarding

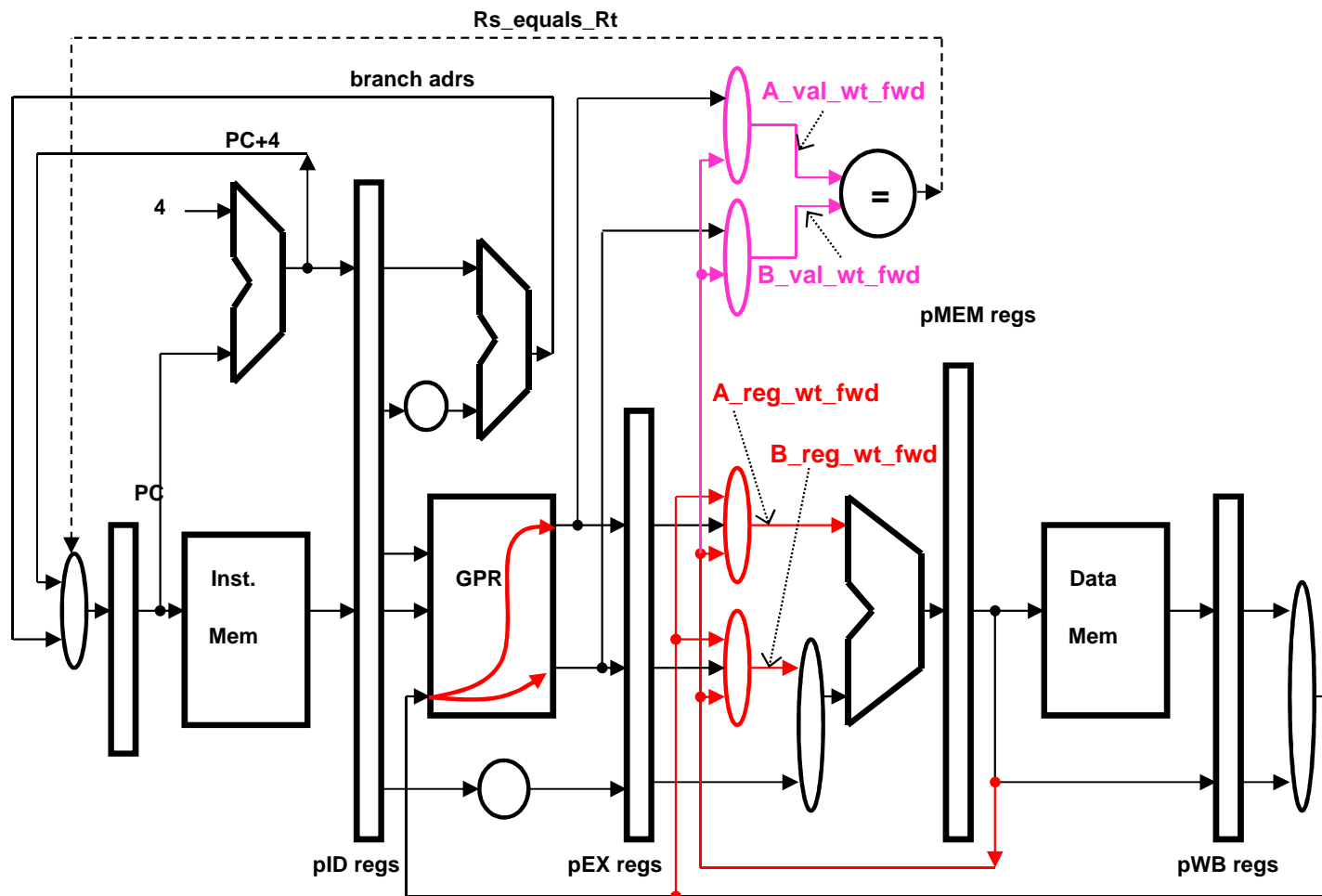


Fig. 8 – MIPS Data Path with Data and Branch Forwarding

You need to add the **magenta** signals

You need to handle also the `jr_address`. To which signal should we connect it to?

All the new signals are listed in page 10 of the BYOC_HW6 doc.

Also in the “empty” vhd file they are already there and marked with “-- @@@HW6”

**Now let's talk on the
Implementation phase**

HW6 MIPS - implementation

1. Take the **HW6_MIPS-empty.vhd** that is similar to the **HW6_MIPS_4sim-empty.vhd** but with all necessary changes to connect the BYOC_Host_Intf to the Nexys2 board circuits and integrate into it all the contents you added to the **HW6_MIPS_4sim.vhd** file in the simulation phase. Then rename it to **HW6_MIPS.vhd**.
2. You should replace the **HW6_Host_Intf_4sim.vhd** with a component that looks the same, the **BYOC_Host_Intf.ngc**, which has the infra-structure that allows the PC to load data into the IMem via the RS232 by the **BYOCInterface** SW.
3. The files we will use to implement the design on the Nexys2 board are:
 - **HW6_MIPS.ucf** - The file listing which signal are connected to which FPGA pins in the Nexys2 board.
 - **HW6_MIPS.vhd** – This is your design of HW5
 - **Fetch_Unit.vhd** - The Fetch Unit you prepared in HW2 after modifications of HW4 & HW6
 - **GPR.vhd** – your GPR File design you prepared in HW3.
 - **dual_port_memory.vhd** – part of the GPR File design you prepared in HW3.
 - **MIPS_ALU.vhd** – your MIPS_ALU design you prepared in HW3 with HW6 modifications
 - **Clock_driver.vhd** – the CK divider & driver.
 - **BYOC_Host_Intf.ngc** - The actual infrastructure interfacing the PC used by HW4_Host_Intf.
4. Now run the Xilinx ISE SW, create a **HW6_MIPS.bit** file and test it on the **Pong1_v32.txt**

**If the game works,
CONGRATULATIONS!!**

**You actually
built your own computer!!!**

Enjoy the assignment!

**Thanks for
listening!**